

EEE Digital Assignment

Regulated Power Supply using Zener Diode

Name: Om Ashish Mishra

Registration Number: 16BCE0789

Slot: L10+L11

Batch: 10(B-Tech Computer Science (Core))

Regulated Power Supply using Zener Diode

AIM:

Setup a power supply using Zener Diode as voltage regulator

APPARATUS REQUIRED:

- Connecting Wires
- Zener Diode(Z5.1)
- Variable power supply(0-12V)
- Resistance of 330Ω and $1k\Omega$
- Voltage of 0-10 mV

CIRCUIT DIAGRAMS:

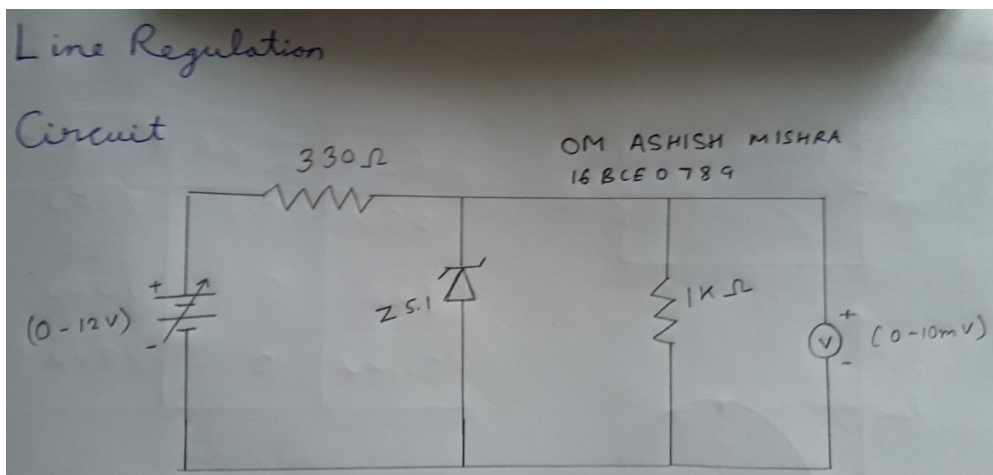


Fig: Line Regulation


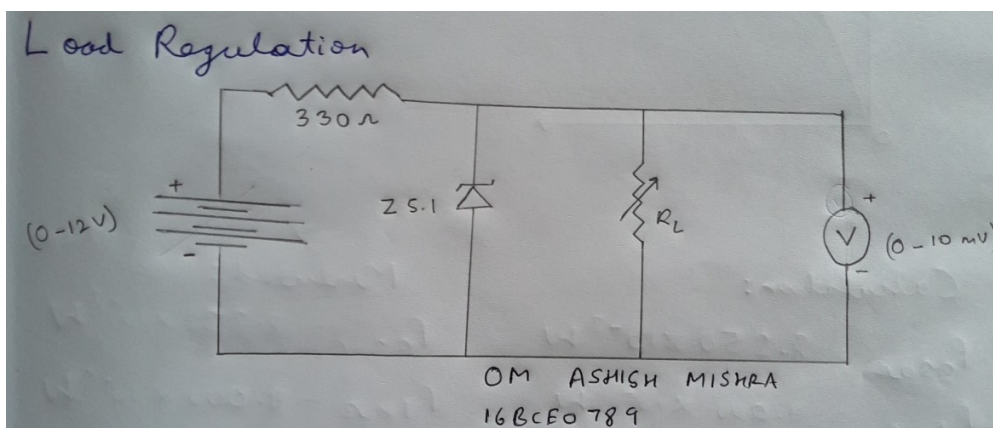


Fig: Load Regulation

PICTURE OF BREADBOARD CONNECTION:

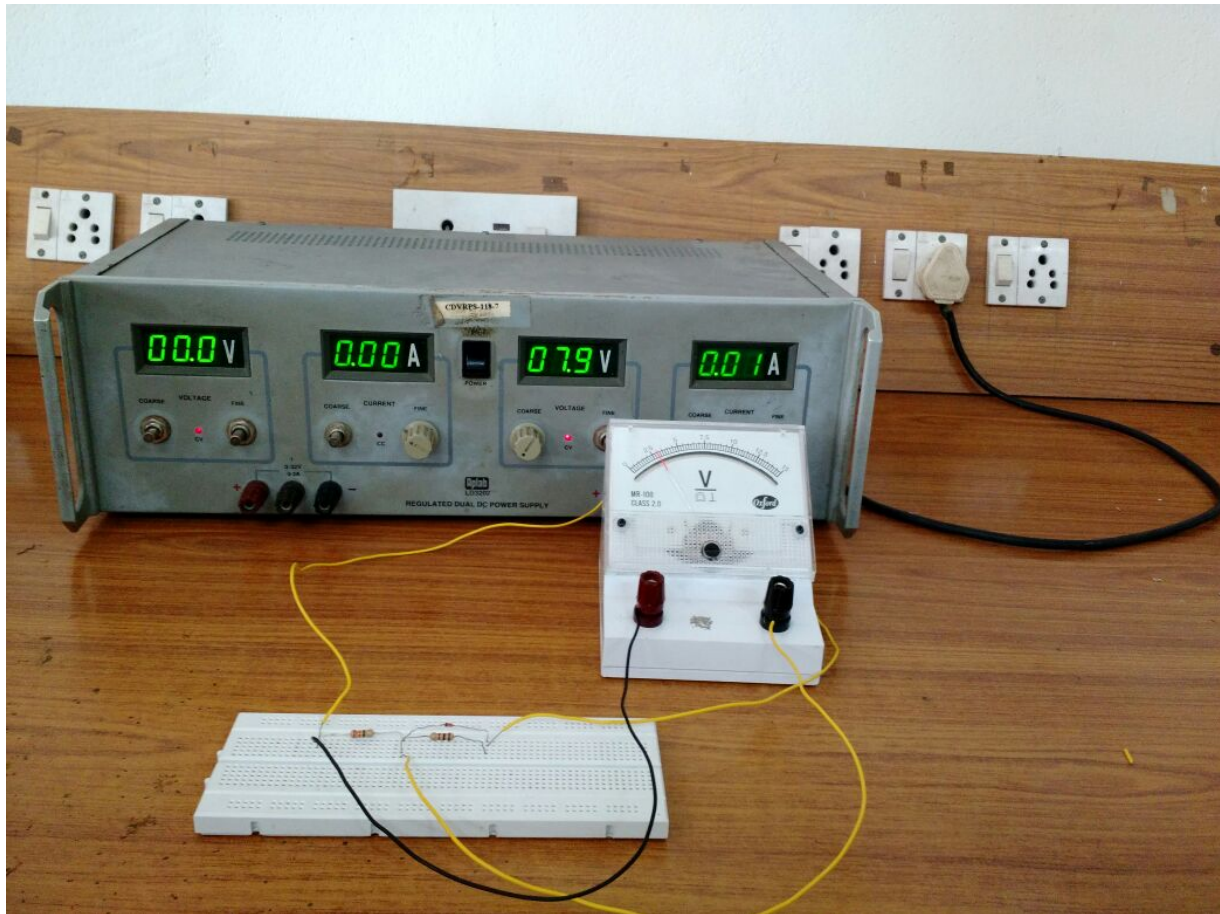

MANUAL CALCULATION(S) / ROUGH WORK:

ROUGH CALCULATION: 16BCE0789

$O/P = V_{out} \times I$	$I/P = V_{in} \times I$	$\eta = \frac{O/P \text{ Power}}{I/P \text{ Power}}$
$1 \times 5 = 5$	$2 \times 5 = 10$	$\eta_1 = \frac{5}{10} = 50\%$
$2.75 \times 5 = 13.75$	$4 \times 5 = 20$	$\eta_2 = \frac{13.75}{20} = 68.75\%$
$3.75 \times 5 = 18.75$	$6 \times 5 = 30$	$\eta_3 = \frac{16.25}{30} = 54.17\%$
$4.25 \times 5 = 21.25$	$8 \times 5 = 40$	$\eta_4 = \frac{21.25}{40} = 53.13\%$
$4.25 \times 5 = 21.25$	$10 \times 5 = 50$	$\eta_5 = \frac{21.25}{50} = 42.50\%$
$4.25 \times 5 = 21.25$	$12 \times 5 = 60$	$\eta_6 = \frac{21.25}{60} = 35.40\%$
$4.25 \times 5 = 21.25$	$14 \times 5 = 70$	$\eta_7 = \frac{21.25}{70} = 30.36\%$

OM ASHISH MISHRA
16BCE0789

GRAPH:

No graph is done for this experiment.

TABULATIONS:

Line Regulation:

V _{in} (V)	V _{out} (V)	V _{330Ω} (V)	I(KEPT CONSTANT)(mA)	O/P (mW)	I/P (mW)
2	1	0.75	5	5	10
4	2.75	1.75	5	13.75	20
6	3.25	2.75	5	16.25	30
8	4.25	3.75	5	21.25	40
10	4.25	4.75	5	21.25	50
12	4.25	5.5	5	21.25	60
14	4.25	7	5	21.25	70

$$\eta = ((o/p \text{ power}) / (i/p \text{ power}))$$

η_1	50%
η_2	68.75%
η_3	54.17%
η_4	53.13%
η_5	42.50%
η_6	35.40%
η_7	30.36%

Load Regulation

R(Ω)	V _o (V)
1000	4.25
2200	4.25
10000	4.25

INFERENCE / RESULT:

In this type of regulation, input voltage is fixed and the load resistance is varying. Output volt remains same, as long as the load resistance is maintained above a minimum value.