

EEE Digital Assignment (Software)

Logic Gates

Name: Om Ashish Mishra

Registration Number: 16BCE0789

Slot: L11+L12

Batch: 10(B-Tech Computer Science (Core))

LOGIC GATES

AIM:

To form primary logic gates using Universal logic gate(NAND).


APPARATUS/TOOL REQUIRED:

ORCAD / PSpice simulator - > 7400 Library – 7408, 7432, 7486, 7404, 7402 & 7400

Simulation Settings: Analysis Type - Time Domain

Run to time - 8ms

CIRCUIT DIAGRAM:

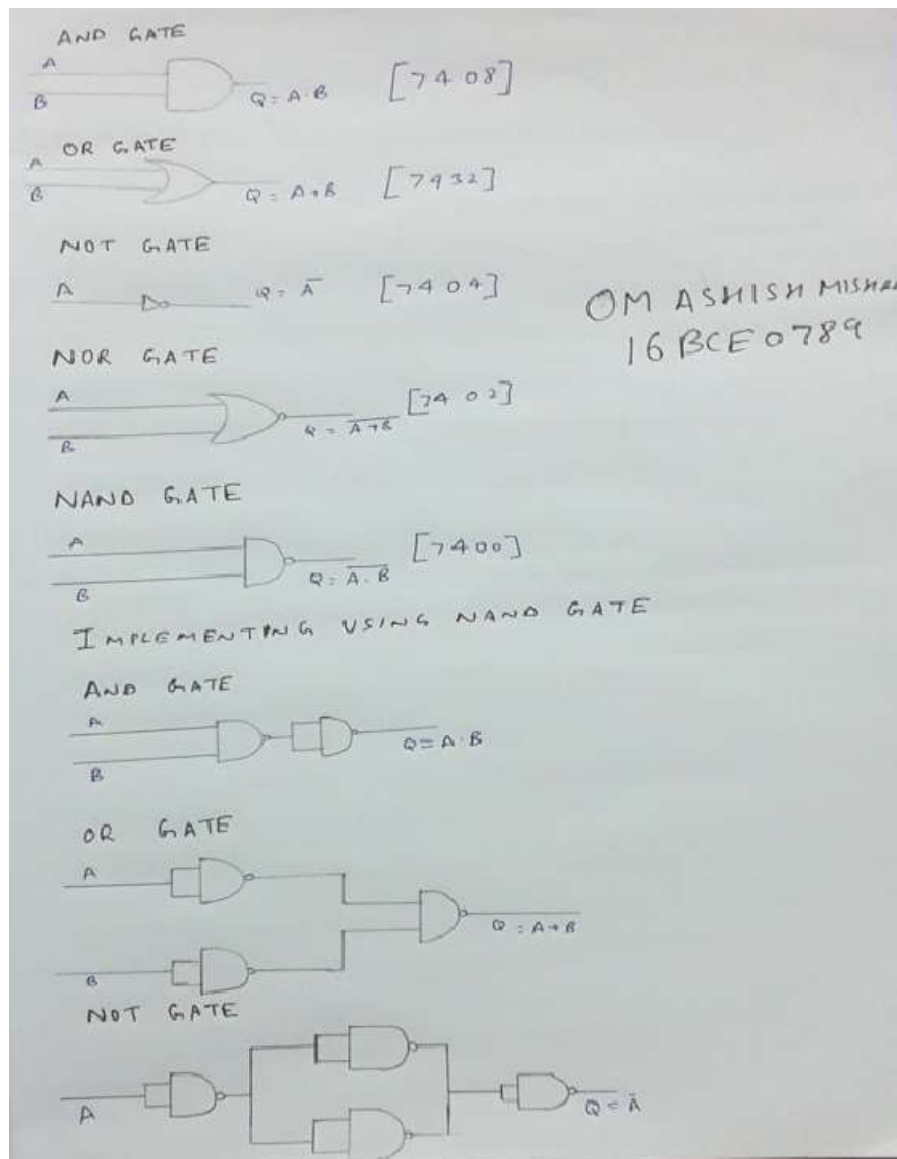

SIMULATION CIRCUIT DIAGRAM:

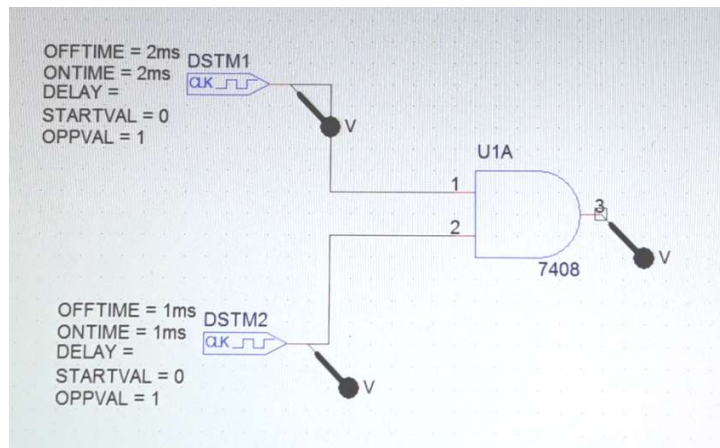


Fig: AND GATE

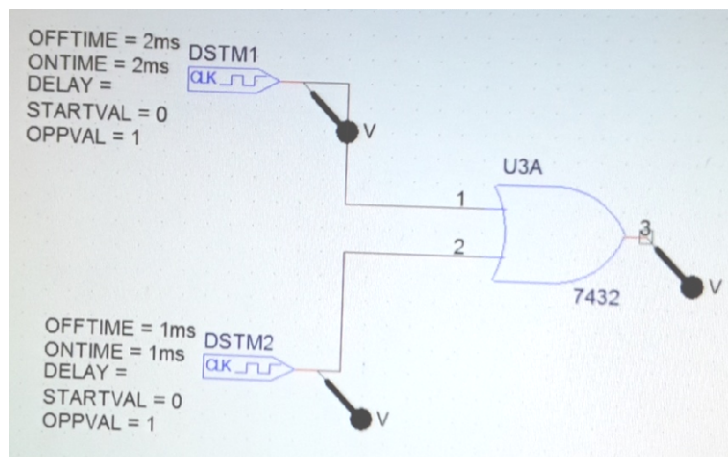


Fig: OR GATE



Fig: NOT GATE



Fig: NAND GATE

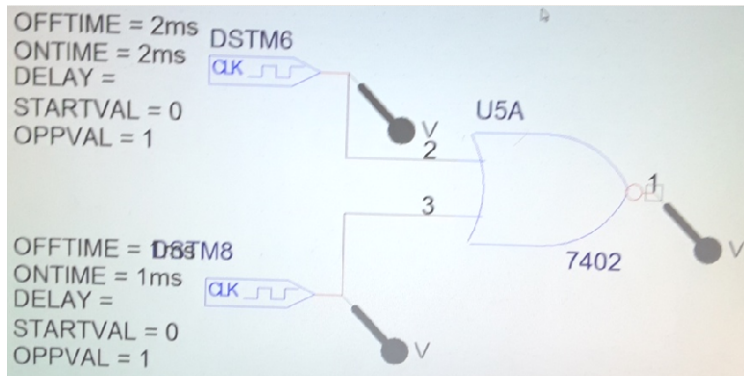


Fig: NOR GATE

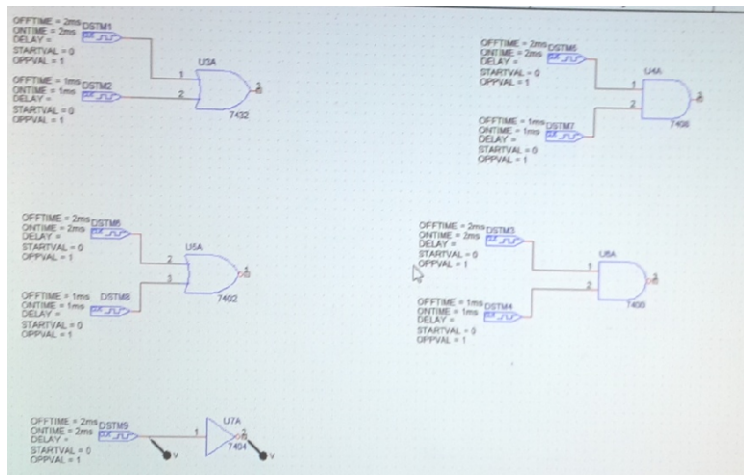


Fig: ALL

 


Fig: AND Using NAND

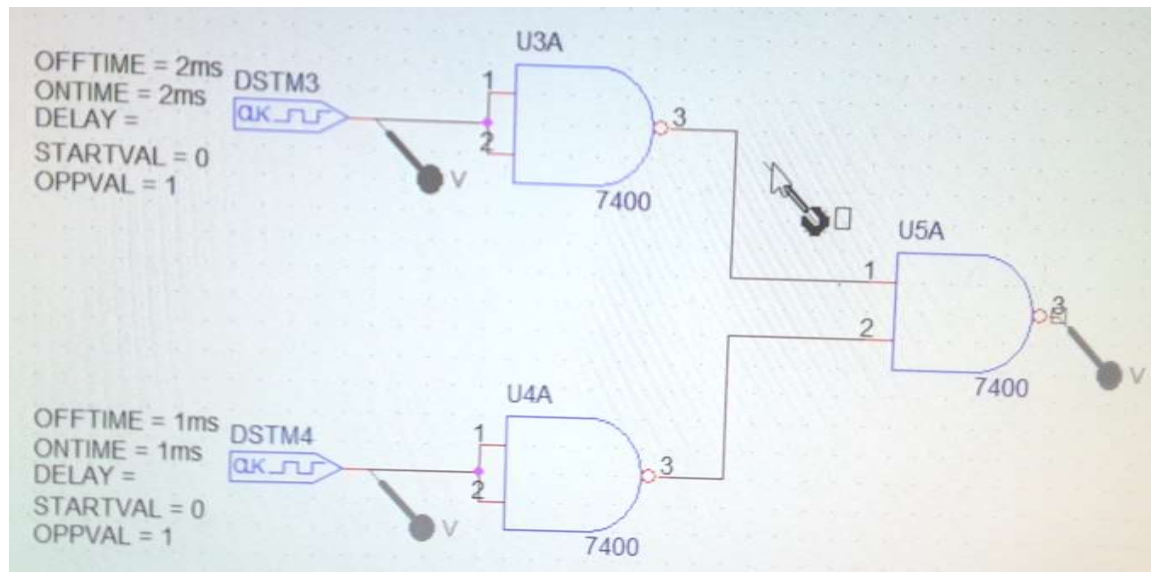


Fig: OR Using NAND

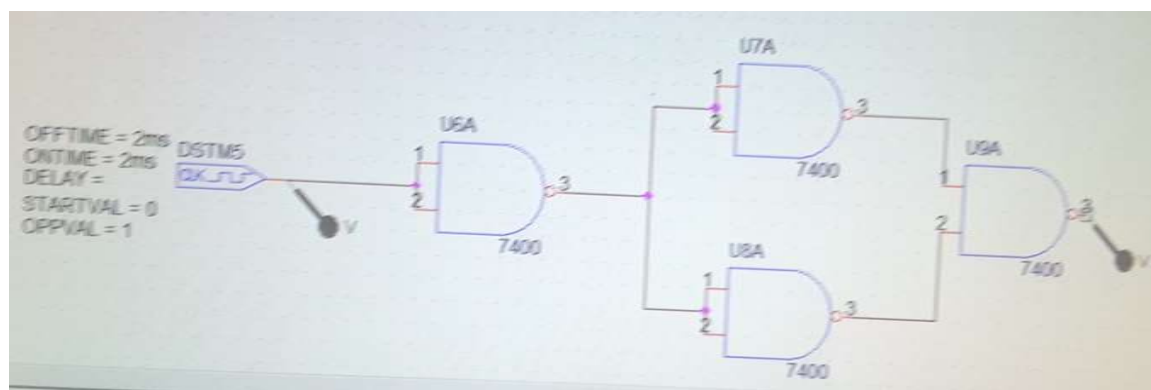

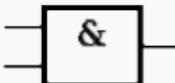

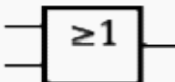

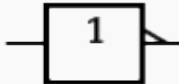



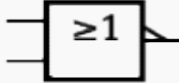


Fig: NOT Using NAND

THEORY:

Type	Distinctive shape (IEEE Std 91/91a-1991)	Rectangular shape (IEEE Std 91/91a-1991 IEC 60617-12 : 1997)	Boolean algebra between A & B	Truth table																		
AND			$A.B$	<table><tr><th colspan="2">INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>A AND B</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	INPUT		OUTPUT	A	B	A AND B	0	0	0	0	1	0	1	0	0	1	1	1
INPUT		OUTPUT																				
A	B	A AND B																				
0	0	0																				
0	1	0																				
1	0	0																				
1	1	1																				
OR			$A+B$	<table><tr><th colspan="2">INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>A OR B</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	INPUT		OUTPUT	A	B	A OR B	0	0	0	0	1	1	1	0	1	1	1	1
INPUT		OUTPUT																				
A	B	A OR B																				
0	0	0																				
0	1	1																				
1	0	1																				
1	1	1																				

NOT			\bar{A}	<table><tr><th colspan="2">NPUT</th><th>OUTPUT</th></tr><tr><td colspan="2">A</td><td>NOT A</td></tr><tr><td colspan="2">0</td><td>1</td></tr><tr><td colspan="2">1</td><td>0</td></tr></table>	NPUT		OUTPUT	A		NOT A	0		1	1		0						
NPUT		OUTPUT																				
A		NOT A																				
0		1																				
1		0																				
NAND			$(A.B)'$	<table><tr><th colspan="2">INPUT</th><th>OUTPUT</th></tr><tr><td>A</td><td>B</td><td>A NAND B</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	INPUT		OUTPUT	A	B	A NAND B	0	0	1	0	1	1	1	0	1	1	1	0
INPUT		OUTPUT																				
A	B	A NAND B																				
0	0	1																				
0	1	1																				
1	0	1																				
1	1	0																				
NOR			$(A+B)'$	<table><tr><th colspan="2">INPUT</th><th>OUTPUT</th></tr><tr><td>A</td><td>B</td><td>A NOR B</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr></table>	INPUT		OUTPUT	A	B	A NOR B	0	0	1	0	1	0						
INPUT		OUTPUT																				
A	B	A NOR B																				
0	0	1																				
0	1	0																				

				1	0	0
				1	1	0

PROCEDURE:

Step 1: Open Capture CIS

Step 2: Click on the File button

Step 3: Click on New Project

Step 4: Select Blank Project

Step 5: Go to Library and click on Sources

Step 6: Select 7400 Library – 7408, 7432, 7486, 7404, 7402&7400

Step 7: Click on New Simulation

Step 8: Analysis Type - Time Domain

Step 9: Run to time – 8 ms (for 2 cycles)

Step 10: Apply it

Step 11: Then we run the simulated program

Step 12: Then we get the graph as the output.

MODEL GRAPH:

 


Fig: AND GATE

 


Fig: OR GATE

 


Fig: NOT GATE

 


Fig: NAND GATE

 


Fig: NOR GATE

 


Fig: AND GATE USING NAND GATE

 


Fig: OR GATE USING NAND GATE

 


Fig: NOT GATE USING NAND GATE

RESULT:

We also learned to use NAND GATE which is one of the Universal Gates and its implementation in formation of AND, OR, NOT Gates.

INFERENCE:

From this experiment we have got a clear picture about the use of different gates(AND,OR,NOT,NAND,NOR).