

# **EEE Digital Assignment**

## **Lamp Dimmer Circuit (Darlington Pair)**

Name: Om Ashish Mishra

Registration Number: 16BCE0789

Slot: L10+L11

Batch: 10(B-Tech Computer Science (Core))

## Lamp Dimmer Circuit (Darlington Pair)



### AIM:

To design a circuit to vary the intensity of the lamp using Darlington pair of BJT.


### APPARATUS REQUIRED:



- A 5V supply
- 2 BJTs of NPN type (Bipolar Junction Transistor)
- A LED (Light Emitting Diode)
- Variable Resistance(POT) of 100 k $\Omega$
- Connecting wires
- A resistance of 330 $\Omega$

### CIRCUIT DIAGRAMS:

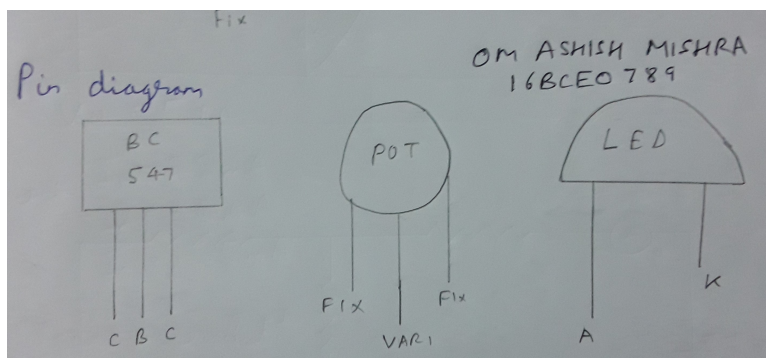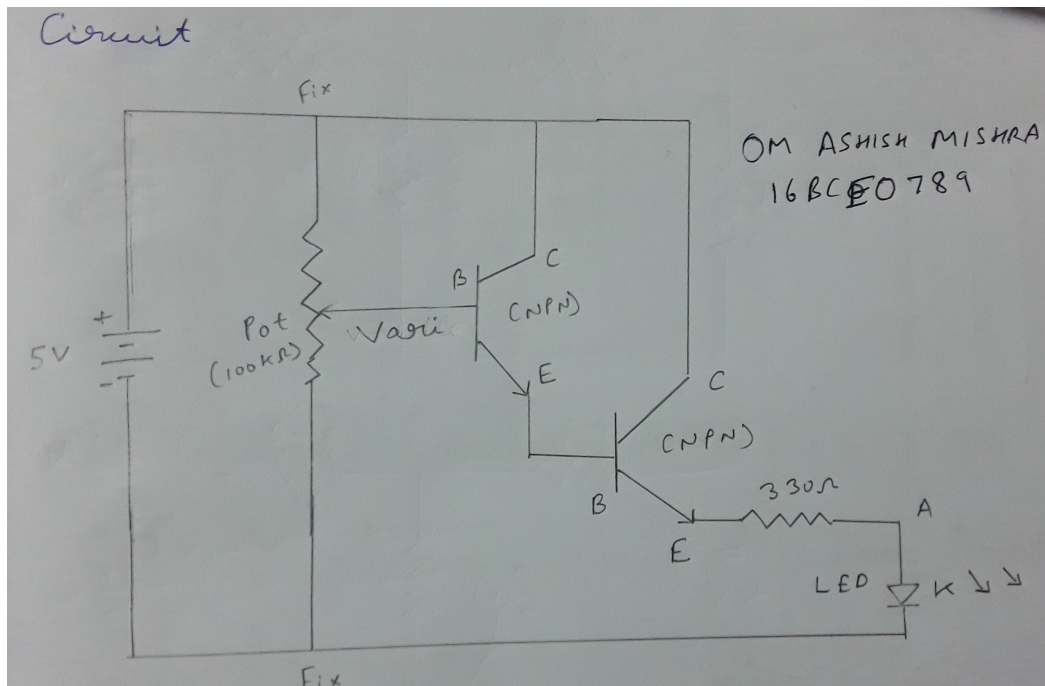


**PICTURE OF BREADBOARD CONNECTION:**

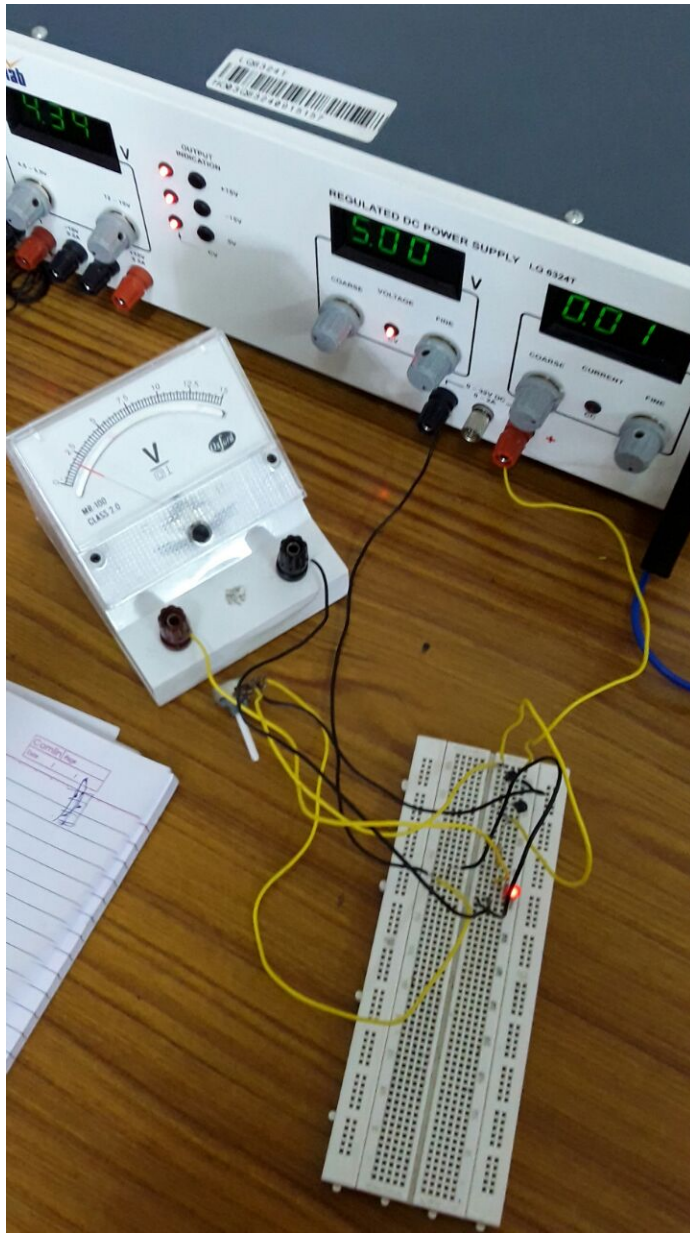

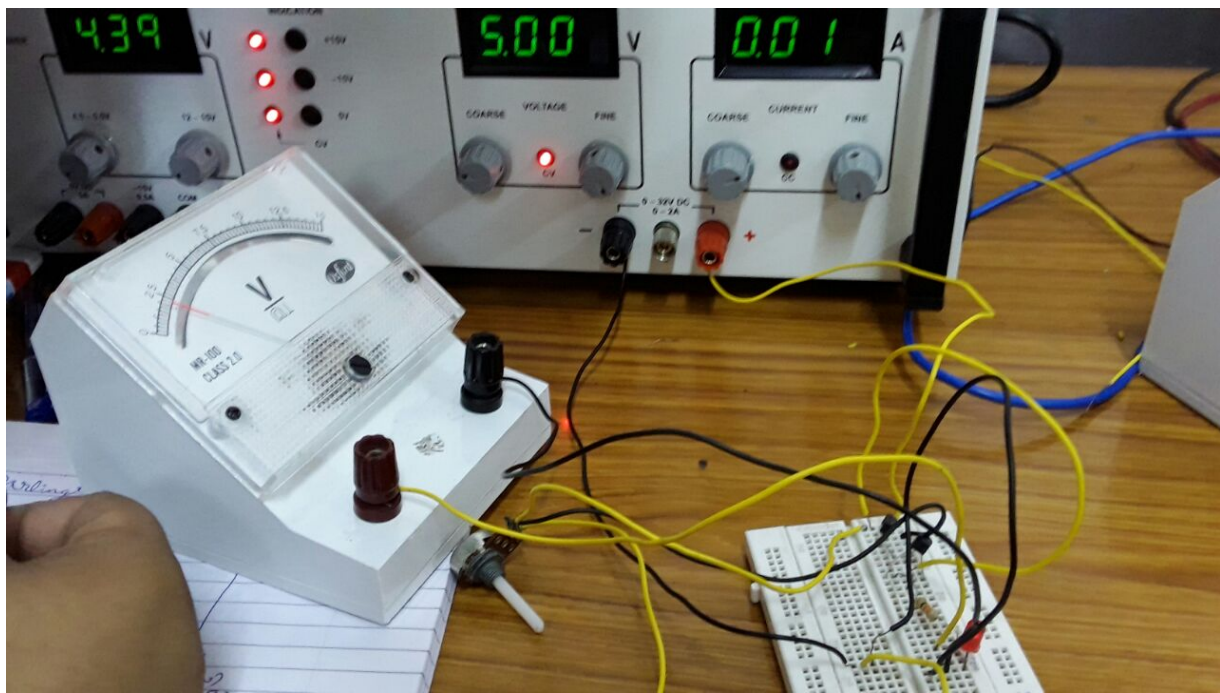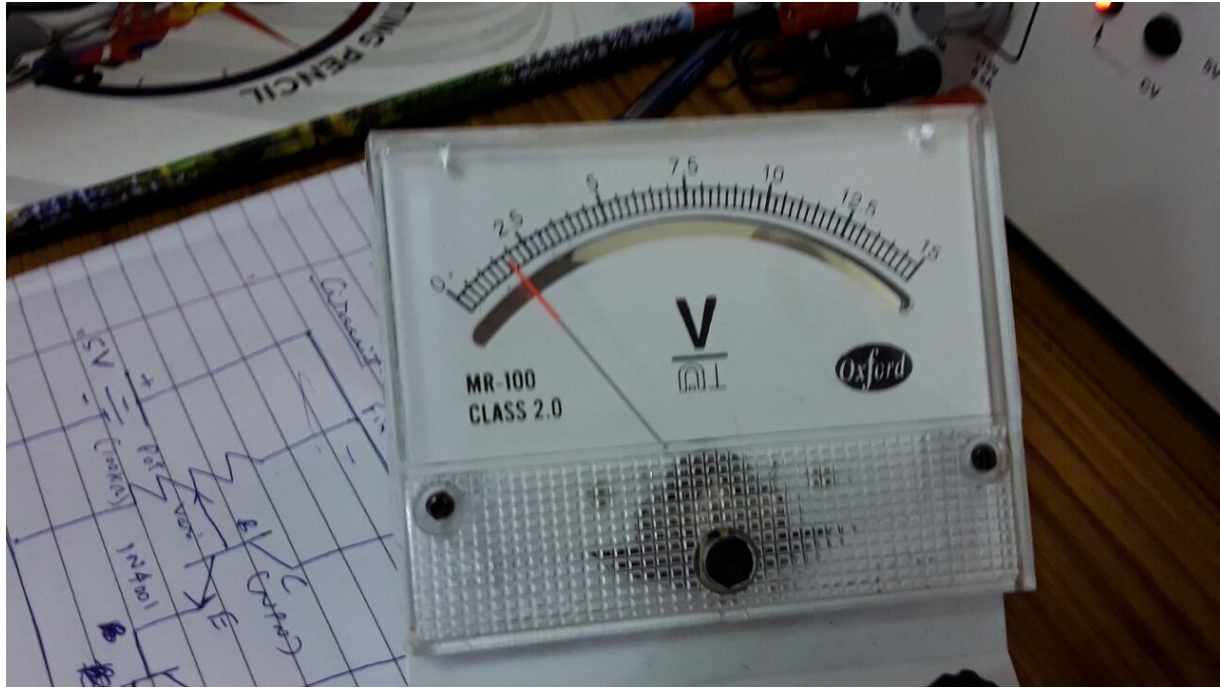



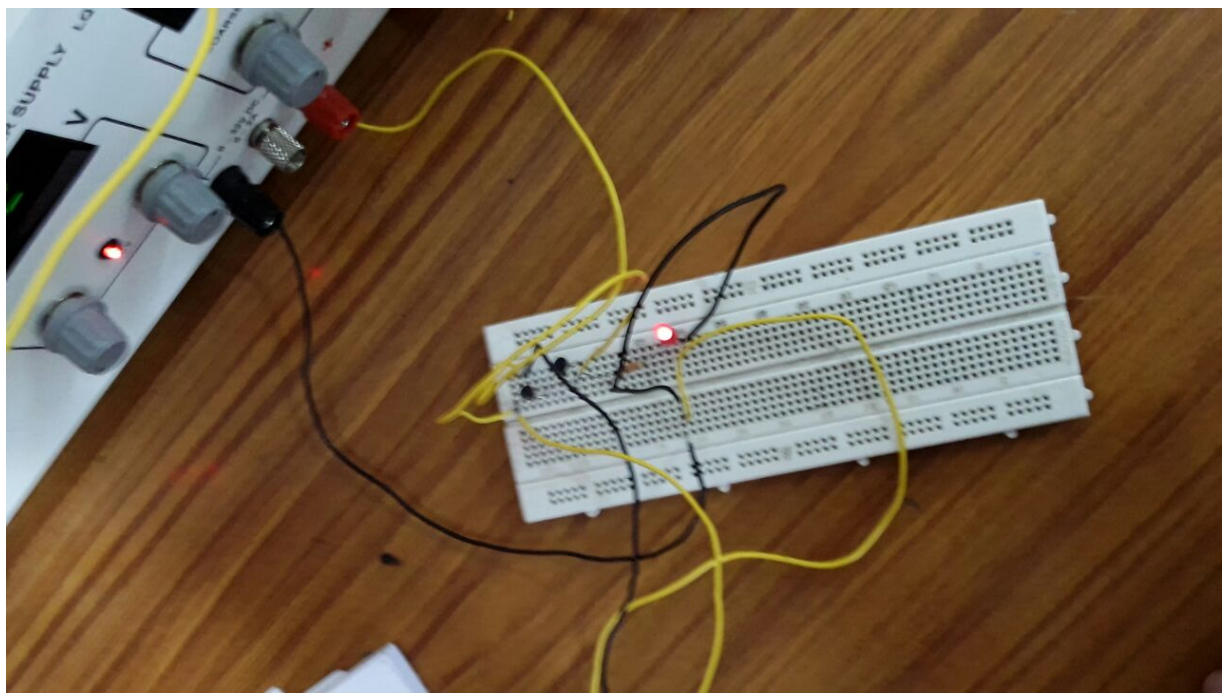

**MANUAL CALCULATION(S) / ROUGH WORK:**

No Manual Calculations were done in this experiment.

**GRAPH:**

No graph has been done for this experiment.

**TABULATION:**

I/P Voltage (V)	O/P Voltage (V)	O/P current (mA)
5	1.75	4.5

OM ASHISH MISHRA  
16 BCE0789

**INFERENCE / RESULT:**

In this experiment we can vary the intensity of the lamp using Darlington pair of BJT. Thus we learn to use BJT, LED and the variable POT resistance.