

EEE Digital Assignment


Name: Om Ashish Mishra

Registration No. : 16BCE0789

Slot: F2

Subject Code: EEE1001

Ans 1:

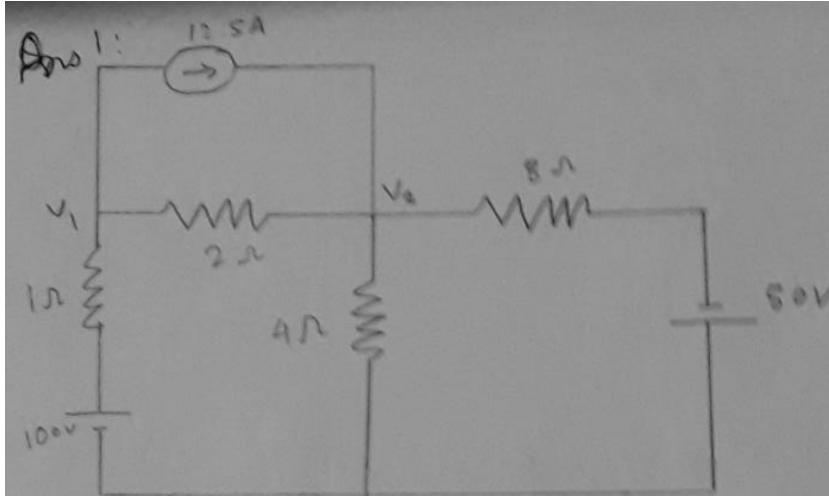

applying nodal analysis.

For V_1 :

$$\frac{V_1 - 100}{1} + \frac{V_1 - V_2}{2} + 12.5 = 0 \rightarrow \textcircled{1}$$

For V_2 :

$$\frac{V_2 - V_1}{2} + \frac{V_2}{4} + \frac{V_2 - 50}{8} - 12.5 = 0 \rightarrow \textcircled{2}$$

\therefore Equation $\textcircled{1}$

$$2V_1 - 200 + V_1 - V_2 + 25 = 0$$

$$\Rightarrow 3V_1 - V_2 = 175$$

$$\Rightarrow V_2 = -175 + 3V_1 \rightarrow \textcircled{3}$$

\therefore Equation $\textcircled{2}$

$$4V_2 - 4V_1 + 2V_2 + V_2 + 50 = 100$$

$$\Rightarrow 7V_2 - 4V_1 = 50$$

$$\Rightarrow 7(-175 + 3V_1) - 4V_1 = 50 \quad (\text{Putting } \textcircled{3} \text{ in the equation})$$

$$\Rightarrow 1225 + 21V_1 - 4V_1 = 50$$

$$\Rightarrow 1275 = 17V_1 \Rightarrow V_1 = 75V$$


Putting the value of V_1 in equation (3) we get:-

$$\begin{aligned} V_2 &= 3 \times 75 - 175 \\ &= 225 - 175 \\ &= 50V \end{aligned}$$

Thus the nodal analysis gives us voltage $V_1 = 75V$
and $V_2 = 50V$

Ans 2:

Ans 2 :

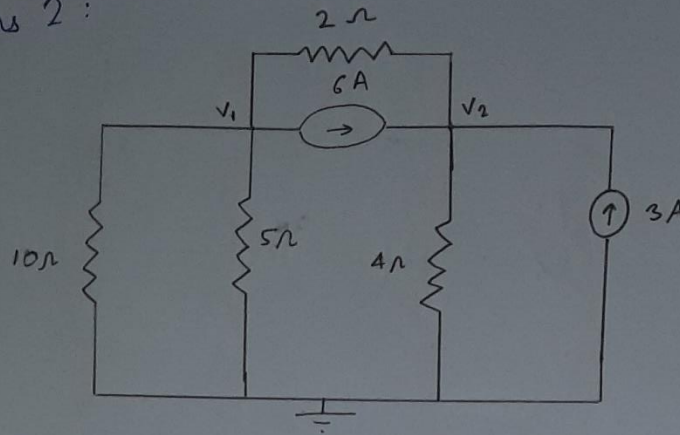

Applying the nodal analysis :

For V_1

$$\frac{V_1 - 0}{10} + \frac{V_1 - 0}{5} + \frac{V_1 - V_2}{2} + 6 = 0$$

$$V_1 + 2V_1 + 5V_1 - 5V_2 + 60 = 0$$

$$8V_1 - 5V_2 + 60 = 0 \rightarrow (1)$$

For V_2

$$\frac{V_2 - V_1}{2} - 6 + \frac{V_2 - 0}{4} - 3 = 0$$

$$3V_2 - 2V_1 - 36 = 0$$

$$3V_2 = 2V_1 + 36$$

$$V_2 = \frac{2V_1 + 36}{3} \rightarrow (2)$$

Putting (2) in (1) :-

$$8V_1 - 5\left(\frac{2V_1 + 36}{3}\right) + 60 = 0$$

$$24V_1 - 10V_1 - 180 + 180 = 0$$


$$V_1 = 0$$

Putting the value of V_1 in (2)

$$V_2 = \left(\frac{2 \times 0 + 36}{3}\right) = 12$$

Thus the nodal analysis gives us voltage $V_1 = 0V$ and $V_2 = 12V$.

Ans 3:

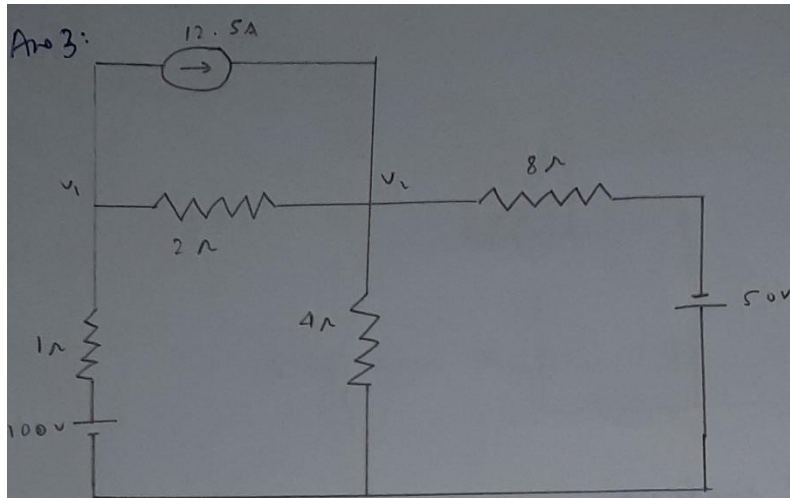

Applying nodal analysis:

For V_1 :

$$\frac{V_1 - 100}{1} + \frac{V_1 - V_2}{2} + 12.5 = 0 \rightarrow (1)$$

For V_2 :

$$\frac{V_2 - V_1}{2} + \frac{V_2}{4} + \frac{V_2 - 50}{8} - 12.5 = 0 \rightarrow (2)$$

Equation (1)

$$2V_1 - 200 + V_1 - V_2 = 25 = 0$$

$$3V_1 - V_2 = 175$$

$$V_2 = -175 + 3V_1 \rightarrow (3)$$

Putting the value V_2 in (2)

$$V_2 = -175 + 3 \times 75$$

$$= -175 + 225$$

$$= 50V$$

Equation (2)

$$4V_2 - 4V_1 + 2V_2 + V_2 + 50 = 100$$

$$7V_2 - 4V_1 = 50$$

$$7(-175 + 3V_1) - 4V_1 = 50$$

$$-1225 + 21V_1 - 4V_1 = 50$$

$$1275 = 17V_1$$

$$V_1 = 75V$$


Thus the nodal analysis gives us voltages $V_1 = 75V$ and $V_2 = 50V$

$$\therefore \text{Current across } 4\Omega = \frac{V_2}{4} = \frac{50}{4} = 12.5A$$

$$V_o = V_2 = 50V$$

Ans 4:

Ans 4:

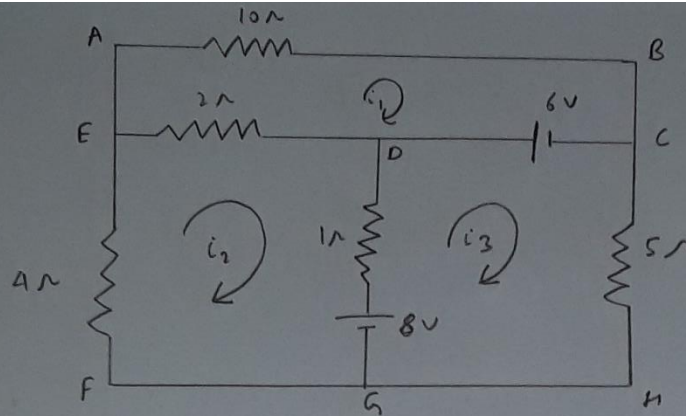

Applying mesh analysis:

In loop EAB CDE :

$$6 - 2(i_1 - i_2) - 10i_1 = 0$$

$$\Rightarrow 12i_1 - 2i_2 = 6$$

$$\Rightarrow 6i_1 - i_2 = 3 \rightarrow \textcircled{1}$$

In loop E D G F E :

$$-8 - 4i_2 - 2(i_2 - i_1) - 1(i_2 - i_3) = 0$$

$$\Rightarrow -8 - 4i_2 - 2i_2 + 2i_1 + i_3 - i_2 = 0$$

$$\Rightarrow 2i_1 - 7i_2 + i_3 = 8 \rightarrow \textcircled{2}$$

In loop DCHG D :

$$-6 - 5i_3 + 8 + (i_2 - i_3) = 0$$

$$i_2 - 6i_3 = -2 \rightarrow \textcircled{3}$$

\therefore Equation one, two, three are :-

$$6i_1 - i_2 + 0i_3 = 3$$

$$2i_1 - 7i_2 + i_3 = 8$$

$$0i_1 + i_2 - 6i_3 = -2$$

Solving the above equations we get :-

$$i_1 = 0.329A \quad i_2 = -1.02A \quad i_3 = 0.16A$$


$$\therefore i = -(i_2 - i_3) = -(1.02 - 0.16)$$

$$\therefore i = -(-1.02 - (-0.16)) A$$

$$= 1.10A$$

Ans: i is 1.1A

Ans 5:

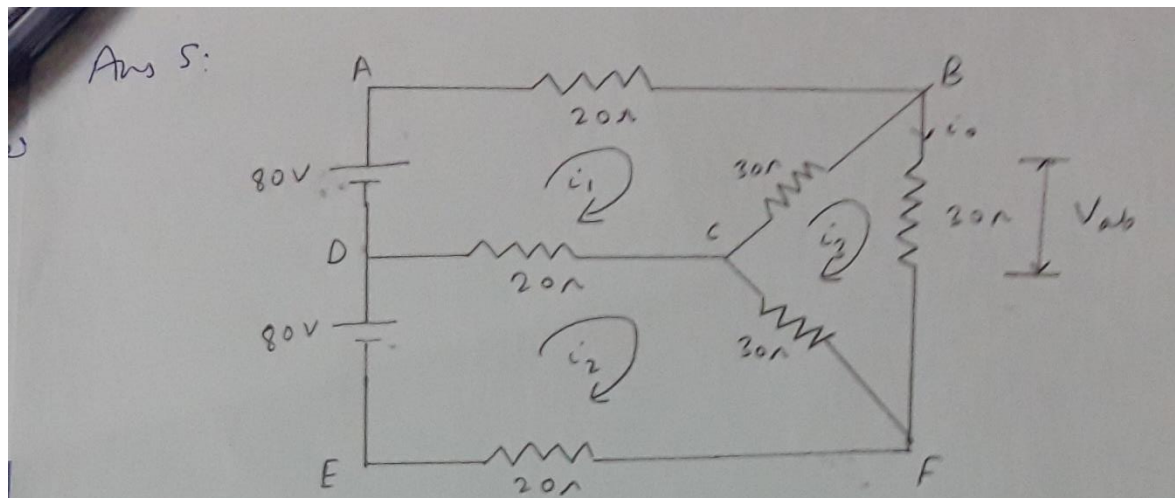

Applying Mesh Analysis:

In loop ABCDA:

$$20 i_1 + 30 (i_1 - i_3) + 20 (i_1 - i_2) = 80$$

$$70 i_1 - 20 i_2 - 30 i_3 = 80 \rightarrow (1)$$

In loop DCFED:

$$30 (i_2 - i_3) + 20 i_2 + 20 (i_2 - i_1) = 80$$

$$-20 i_1 + 70 i_2 - 30 i_3 = 80 \rightarrow (2)$$

In loop BCFB:

$$30 (i_3 - i_1) + 30 i_3 + 30 (i_3 - i_2) = 0$$

$$-30 i_1 - 30 i_2 + 90 i_3 = 0 \rightarrow (3)$$

Solving equations (1), (2), (3) we get:-

$$i_1 = 2.666 \approx 2.67 \text{ A}$$

$$i_2 = 2.666 \approx 2.67 \text{ A}$$


$$i_3 = 1.777 \approx 1.78 \text{ A}$$

$$\therefore i_3 = i_0 = 1.78$$

$$\therefore V_{ab} = i_0 \times R = 1.78 \times 30 = 53.4 \text{ V}$$

Ans 6:

Ans 6:

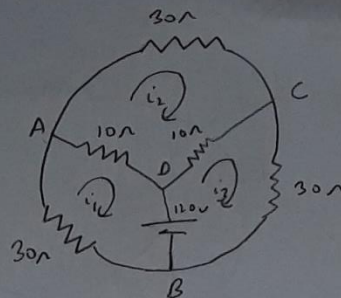

Applying Mesh analysis:

In loop A P B A :

$$-120 - 30 i_1 - 10 (i_1 - i_2) = 0$$

$$\Rightarrow -40 i_1 + 10 i_2 = 120$$

$$\Rightarrow -4 i_1 + i_2 = 12 \rightarrow \textcircled{1}$$

In loop A D C A :

$$30 i_2 + 10 (i_2 - i_3) + 10 (i_2 - i_1) = 0$$

$$\Rightarrow 50 i_2 = 10 i_1 + 10 i_3$$

$$\Rightarrow i_1 - 5 i_2 + i_3 = 0 \rightarrow \textcircled{2}$$

In loop D C B D :

$$120 - 10 (i_3 - i_2) - 30 i_3 = 0$$

$$120 = 40 i_3 - 10 i_2$$

$$-i_2 + 4 i_3 = 12 \rightarrow \textcircled{3}$$

\therefore The equations $\textcircled{1}$, $\textcircled{2}$, $\textcircled{3}$:

$$-4 i_1 + i_2 + 0 i_3 = 12$$

$$i_1 - 5 i_2 + i_3 = 0$$


$$0 i_1 - i_2 + 4 i_3 = 12$$

Solving the above equations we get :


$$i_1 = -3A \quad i_2 = 0A \quad i_3 = 3A$$

Ans 7:

Ans 7:

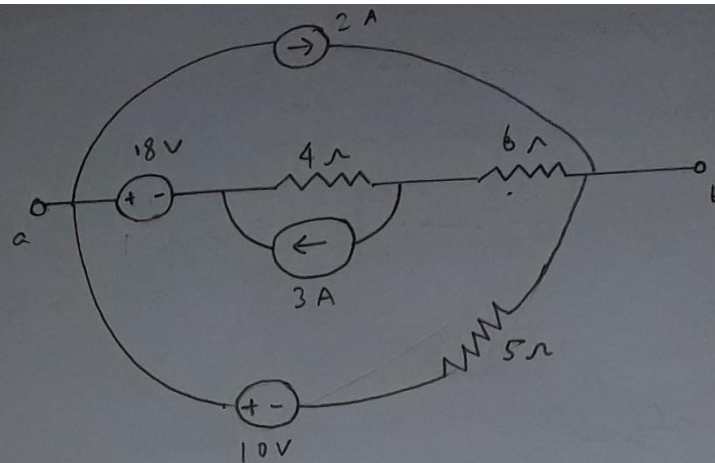

By using source transformation :

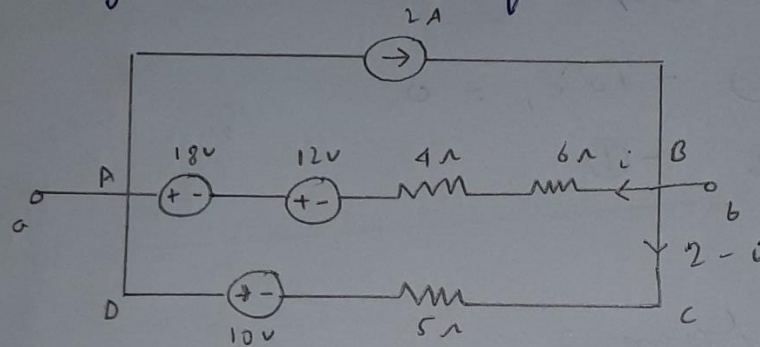

Using KVL in loop ABCDA :

$$12 + 18 - 10 + 5(2 - i) - 10i = 0$$

$$\Rightarrow -10i + 30 - 10 + 10 - 5i = 0$$

$$\Rightarrow -15i = -30$$

$$\Rightarrow i = 2A$$


$$V_{ab} = V_{Th} = -4i - 6i + 12 + 18$$

$$= -10i + 30$$

$$= 30 - 10(2)$$


$$= 10V$$

Ans 8:

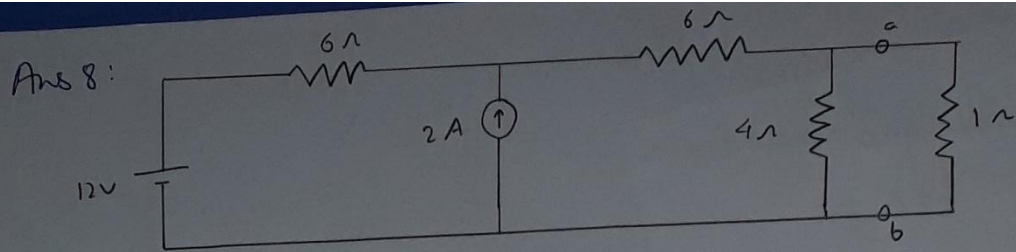


for R_{th} :

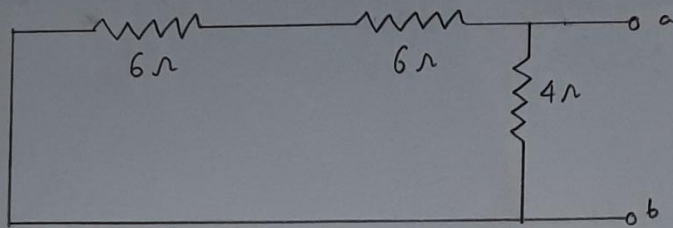We have to short circuit the voltage source and make an open circuit for current source



$$R_{th} = \frac{(6+6) \times 4}{(6+6) + 4} = \frac{12 \times 4}{16} = 3 \Omega$$

for V_{th} :

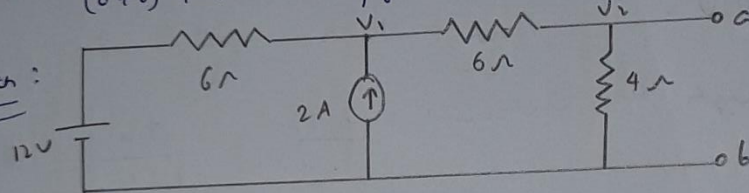

Applying Nodal Analysis:

At V_1

$$\frac{V_1 - 12}{6} + \frac{V_1 - V_2}{6} = 2$$

$$\Rightarrow 2V_1 - V_2 = 24 \rightarrow (1)$$

At V_2

$$\frac{V_2 - V_1}{6} + \frac{V_2}{4} = 0$$

$$5V_2 - 2V_1 = 0$$


$$V_1 = \frac{5V_2}{2} \rightarrow (2)$$

From (1) & (2)

$$V_2 = 6V$$

$$\therefore V_{th} = 6V$$


\therefore The Thevenin's circuit is:

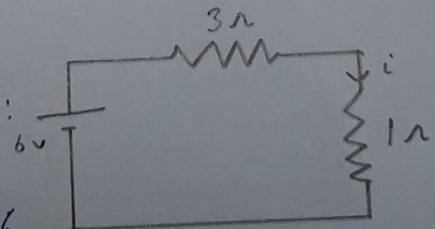


$$I = \frac{V_{th}}{R_{th} + R_L} = \frac{6}{3+1} = \frac{6}{4} = 1.5A$$

Ans 9:


Ans 9:

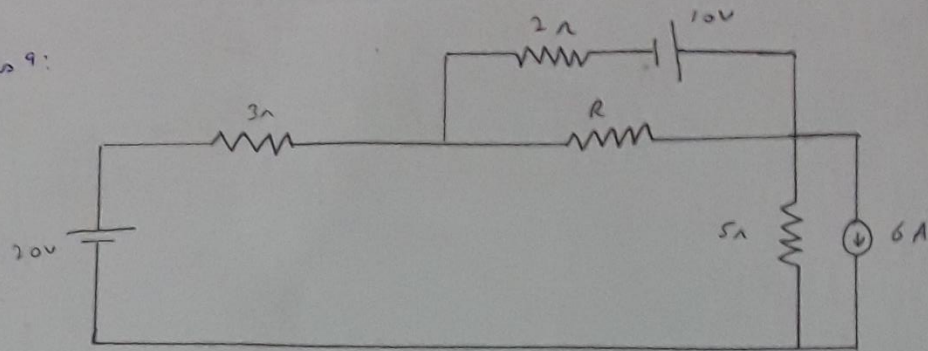

Using source transformation:

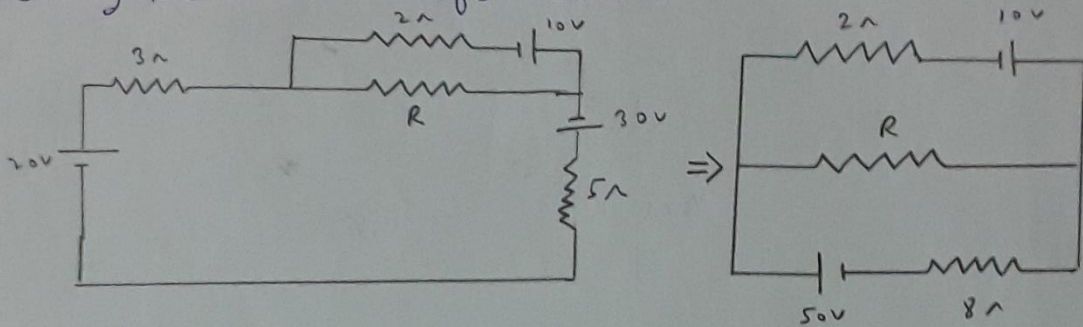

For R_{th}

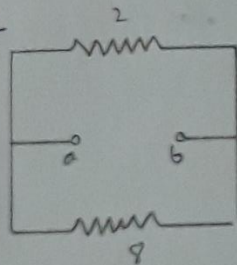

$$R_{th} = \frac{2 \times 8}{8 + 2} = \frac{16}{10} = 1.6 \Omega$$

For V_{th}


We can see the current coming out of a is back to b in two paths (one of 2Ω resistance and other of 8Ω resistance).

$$\therefore \frac{E_{th}}{1.6} = \frac{10}{2} + \frac{50}{8} = 5 + 6.25 = 11.25$$



$$E_{th} = 11.25 \times 1.6 = 18 V$$

$$\text{Max power delivered to } R = \frac{(18)^2}{4 \times 1.6} = 50.625 W$$

Ans 10:

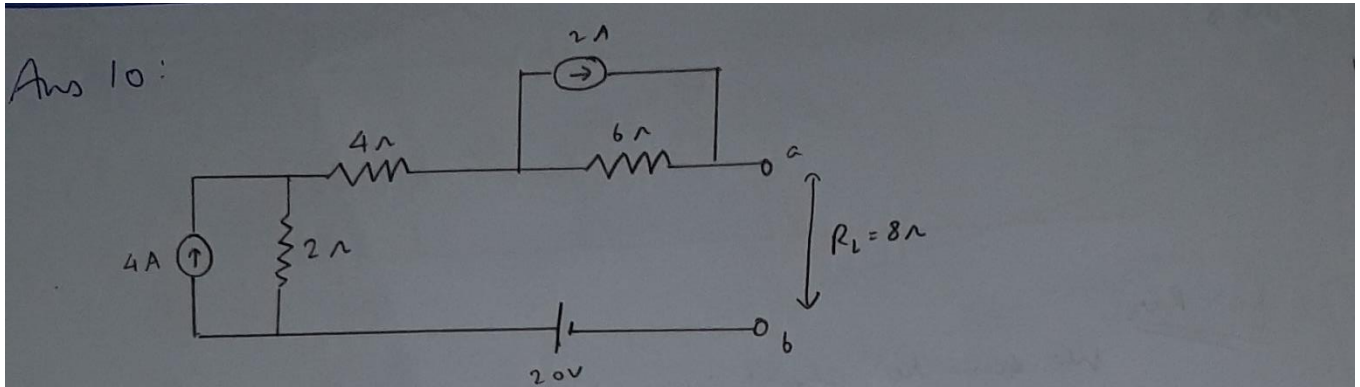

Applying source transformation:

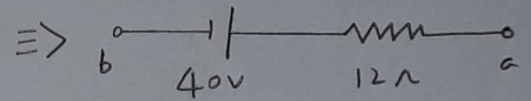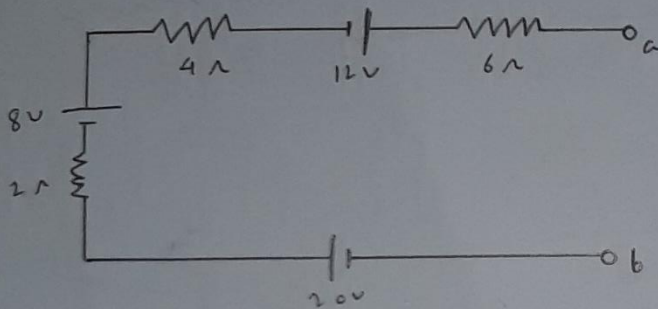

$$\therefore V_{th} = 40V \quad R_{th} = 12\Omega \quad R_L = 8\Omega$$

$$\therefore I \text{ through the circuit} = \frac{40}{R_L + R_{th}} = \frac{40}{8 + 12} = 2A$$

Now for maximum power

$$R_L = R_{th} \quad \therefore R_L = 12\Omega$$

$$\begin{aligned} \text{Thus, the maximum power} &= \frac{V_{R_L}^2}{4R_L} = \frac{40 \times 40}{4 \times 12} \\ &= 33.33W \end{aligned}$$